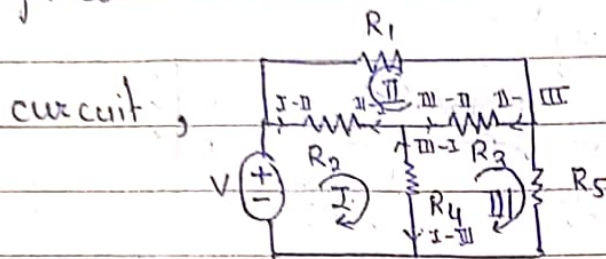


Q3

Problem Statement,

using kirchhoff's voltage law to derive set of equations for finding current for circuit. with the help of gauss-seidel method.



given, $R_1 = 6 \Omega$

$\text{I} \Rightarrow i_1$

$R_2 = 4 \Omega$

$\text{II} \Rightarrow i_2$

$R_3 = 8 \Omega$

$\text{III} \Rightarrow i_3$

$R_4 = 2 \Omega$

$R_5 = 5 \Omega$

$V = 20V$

assumptions,

the system is ideal, and there is no energy loss in heat.

there is no resistance in wire.

$$V = (i_1 - i_2) R_2 + (i_1 - i_3) R_4 \quad \text{--- for (I)}$$

$$0 = (i_3 - i_1) R_4 + (i_3 - i_2) R_3 + i_3 R_5 \quad \text{--- for (II)}$$

$$0 = (i_2 - i_3) R_3 + (i_2 - i_1) R_2 + i_2 R_1 \quad \text{--- for (III)}$$

$$20 = 4i_1 - 4i_2 + 2i_1 - 2i_3$$

$$20 = 6i_1 - 4i_2 - 2i_3 \quad \text{--- (I)}$$

$$0 = 8i_2 - 8i_3 + 4i_2 - 4i_1 + 6i_2$$

$$0 = -4i_1 + 18i_2 - 8i_3 \quad \text{--- (II)}$$

$$0 = 2i_3 - 2i_1 + 8i_3 - 8i_2 + 5i_3$$

$$0 = -2i_1 - 8i_2 + 15i_3 \quad \text{--- (III)}$$

$$i_1 = \frac{1}{6} (20 + 4i_2 + 2i_3)$$

$$i_2 = \frac{1}{18} (4i_1 + 8i_3)$$

$$i_3 = \frac{1}{15} (2i_1 + 8i_2)$$

\Rightarrow iteration initial $i_1^0 = 0$ $i_2^0 = 0$ $i_3^0 = 0$

$$i_1^1 = \frac{1}{6} (20 + 0 + 0) \quad i_2^1 = \frac{1}{18} (4(i_1^1) + 0) \quad i_3^1 = \frac{1}{15} (2i_1^1 + 8i_2^1)$$

$$= \frac{1}{18} \left(4 \left(\frac{20}{6} \right) \right) \quad i_3^1 = \frac{1}{15} \left(2i_1^1 + \frac{2 \times 8i_1^1}{9} \right)$$

\Rightarrow II iteration

$$i_1^2 = \frac{1}{6} (20 + 4i_2^1 + 2i_3^1)$$

$$i_2^2 = \frac{1}{18} (4i_1^2 + 8i_3^1)$$

$$i_3^2 = \frac{1}{15} (2i_1^2 + 8i_2^2)$$

$$\begin{bmatrix} 6 & -4 & -2 \\ -4 & 18 & -8 \\ -2 & -8 & 15 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \\ 0 \end{bmatrix}$$

$$\underline{i_1 \quad i_2 \quad i_3} \Rightarrow \underline{5 \quad 2 \quad 2}$$

$$i_1 = 5.175879 \approx 5$$

$$i_2 = 1.909547 \approx 2$$

$$i_3 = 1.708542 \approx 2$$