

(A4) Problem Statement :

Using Euler's method, compute current and charge by solving the following pair of equations within time interval 0 to 0.1 sec with a step size of 0.01 sec with the help of following parameters

(i) initial current ($i(0)$) = 0

(ii) initial charge ($q(0)$) = 1C

(iii) inductance (L) = 5H

(iv) resistance (R) = 200Ω

(v) capacitance (C) = 10^{-4} F

equations, $iR + L \frac{di}{dt} + \frac{q}{C} = 0$ and,

$$\frac{dq}{dt} = i$$

knowns,

$i(0) = 0$ (initial current)

$q(0) = 1C$ (initial charge)

$L = 5H$ (inductance)

$R = 200\Omega$ (resistance)

$C = 10^{-4}F$ (capacitor)

$t \in [0, 0.1]$ sec (time interval)

$h = \Delta t = 0.001$ sec (step size)

unknowns,

$i(t) = ?$ where $t \in [0, 0.1]$

(current at time (sec) within t and stepsize 0.001 sec)

$q(t) = ?$ where $t \in [0, 0.1]$

(~~current~~ at time (sec) within t and stepsize 0.001 sec)
charge

Solⁿ: $iR + L \frac{di}{dt} + \frac{q}{C} = 0$ and $\frac{dq}{dt} = i$ — given

$(i_0)' = \left(-\frac{q}{C} - iR \right) \frac{1}{L}$ and $(q_0)' = i_0$

$(i_0)' = \left(-\frac{1}{10^{-4}} - 0(200) \right) \frac{1}{5}$ and $(q_0)' = 0$

$V_{i+1} = V_i + h f(V_i)$ — from euler's method.

(i) $i_1 = i_0 + h f(i_0)$
 $= 0 + (0.001) \left[\frac{1}{5} \left(-\frac{1}{10^{-4}} - 0 \right) \right]$
 $= 0.001 \times \left(-\frac{10000}{5} \right)$
 $= -20 \text{ amp}$

(ii) $q_1 = q_0 + h f(q_0)$
 $= 1 + (0.001)(0)$
 $= 1C$

assumptions,

① System behave as ideal (circuit, etc)

Current and Charge in RLC Circuit Over Time

